

Design Name : Sequence of pre-recorded outputs.

Objective :

Learn how to design a circuit in order to generate the required output sequence.

Assignment :

Assume that we have an array of `STD_LOGIC_VECTOR(7 downto 0)` elements. Each vector indicate which LEDs are on and/or off. The vectors are output one by one with one second intervals. For example, if the array is
("01010101" , "11111111" , "00000000" , ...)
then at first second 01010101 pattern will be seen on the LEDs, and at the 2nd second all LEDs will be lit, at third all will be off and so on. The sequence will start over again when finished.

1. Design the circuit that does that. This may just be a counter. Output is the array element indexed by the counter. Array size should be used automatically.
2. Make the vector size 12 bits, where first 4 bits indicate the number of seconds it will wait before moving to the next 12-bit word.

Follow Up Work :

Modify your design so that it will accept a reset input.

Modify the design so that it accepts an additional input and jumps to Mth word when this input is given. Determine constant M as you wish (it should be less than the size of the array of course)

Homework :

Modify the design so that it will accept 4 additional inputs. Also, make the vector sizes 12 bits, 8 of which still controls the LEDs, but high 4 bits work in conjunction with these inputs. If the inputs and these 4 bits are same then the jump occurs.