

# Sequencing



by Erol Seke

For the course “`Introduction to VHDL`”



  
# Key Bounce

Making or opening circuits in mechanical switches take a finite amount of time



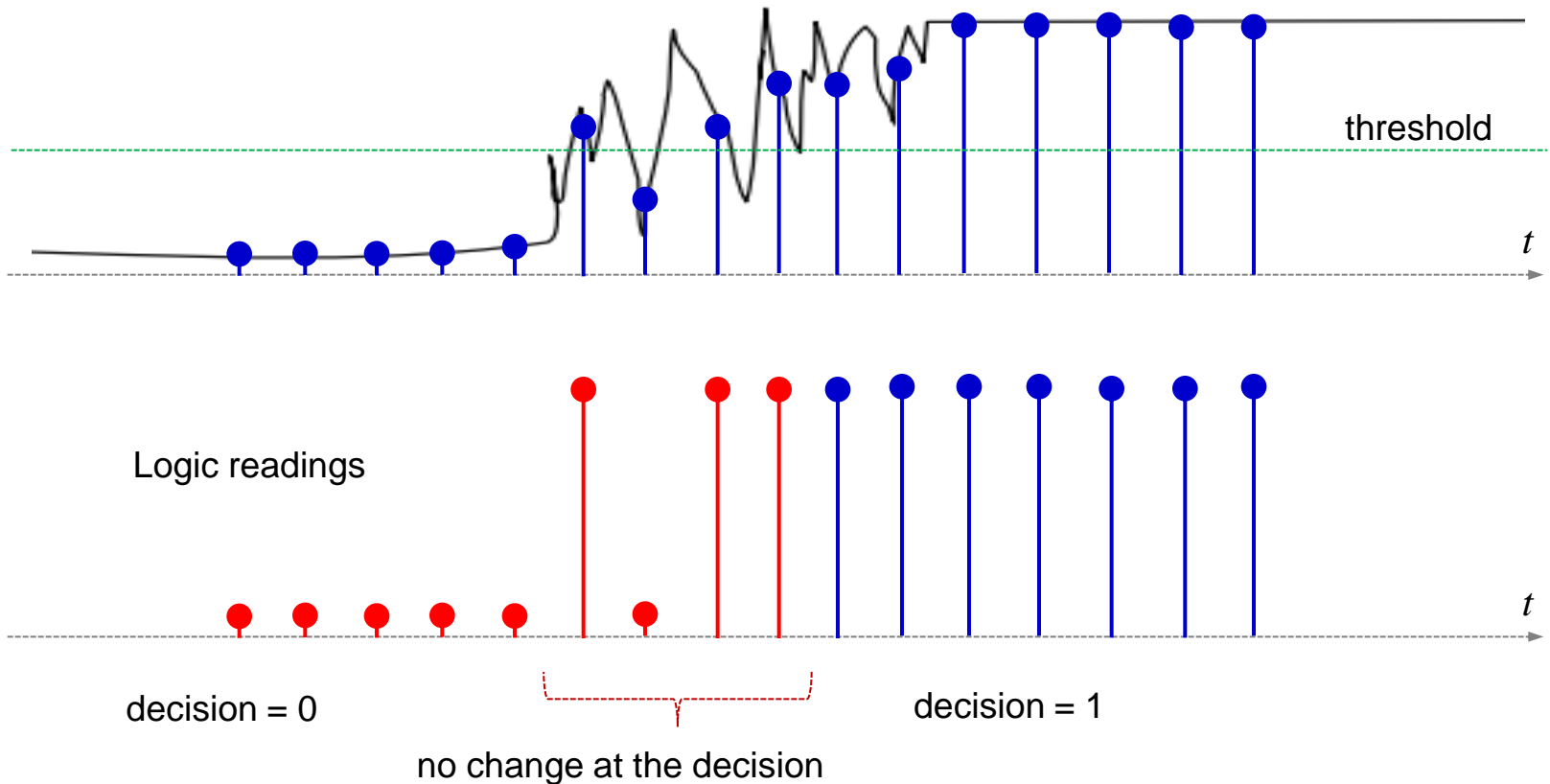
## Simple Digital Solution

Measure the logic input 3 times with approximately 5 ms apart.  
If all 3 are the same then set the output (decision) to that value.




Note : 5 ms is not decisive. It really depends on the mechanical characteristics of the contacts.  
It can be from 2 ms upto 50 ms.

# Debouncer Circuit

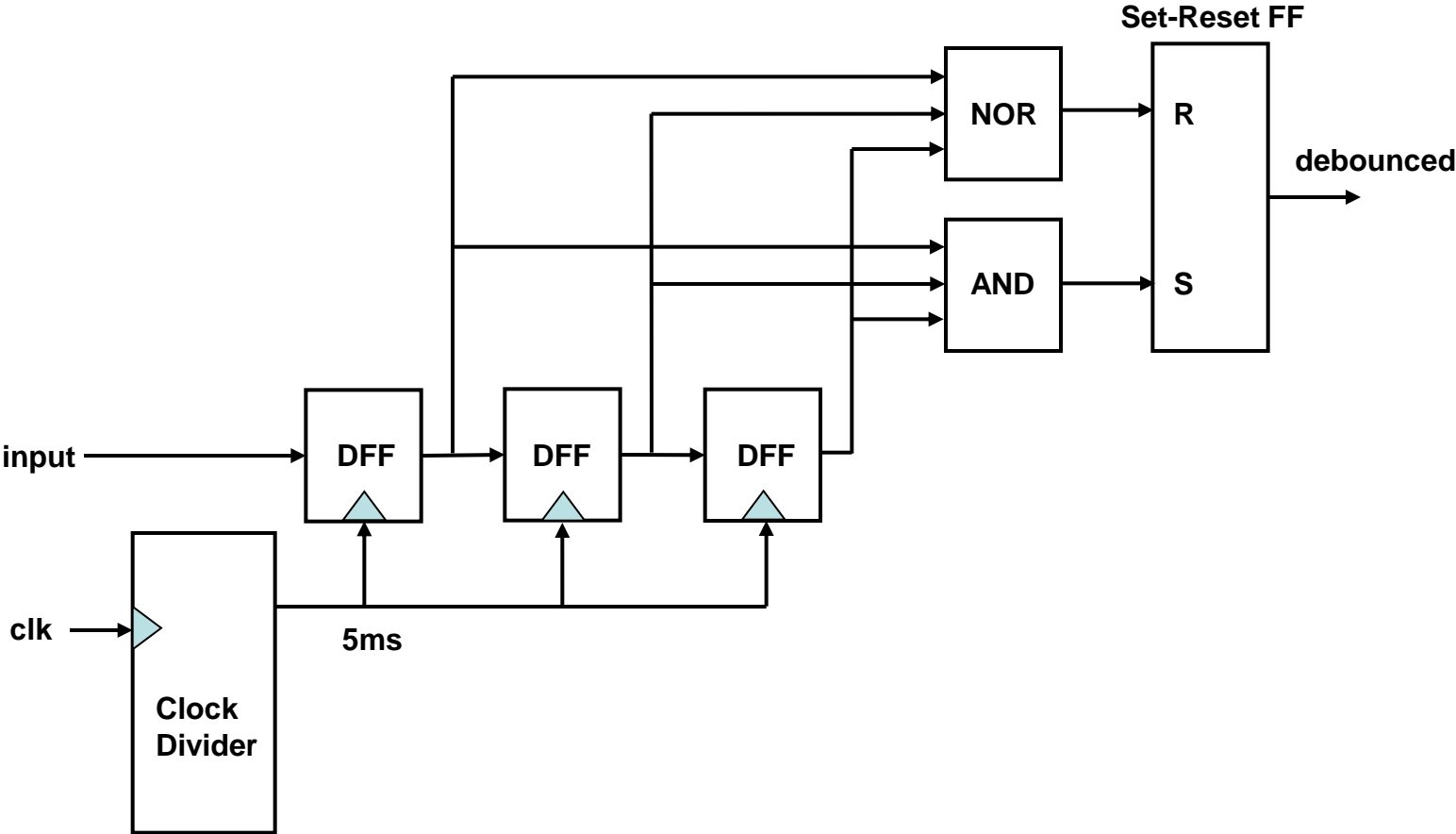

# Sliding LEDs

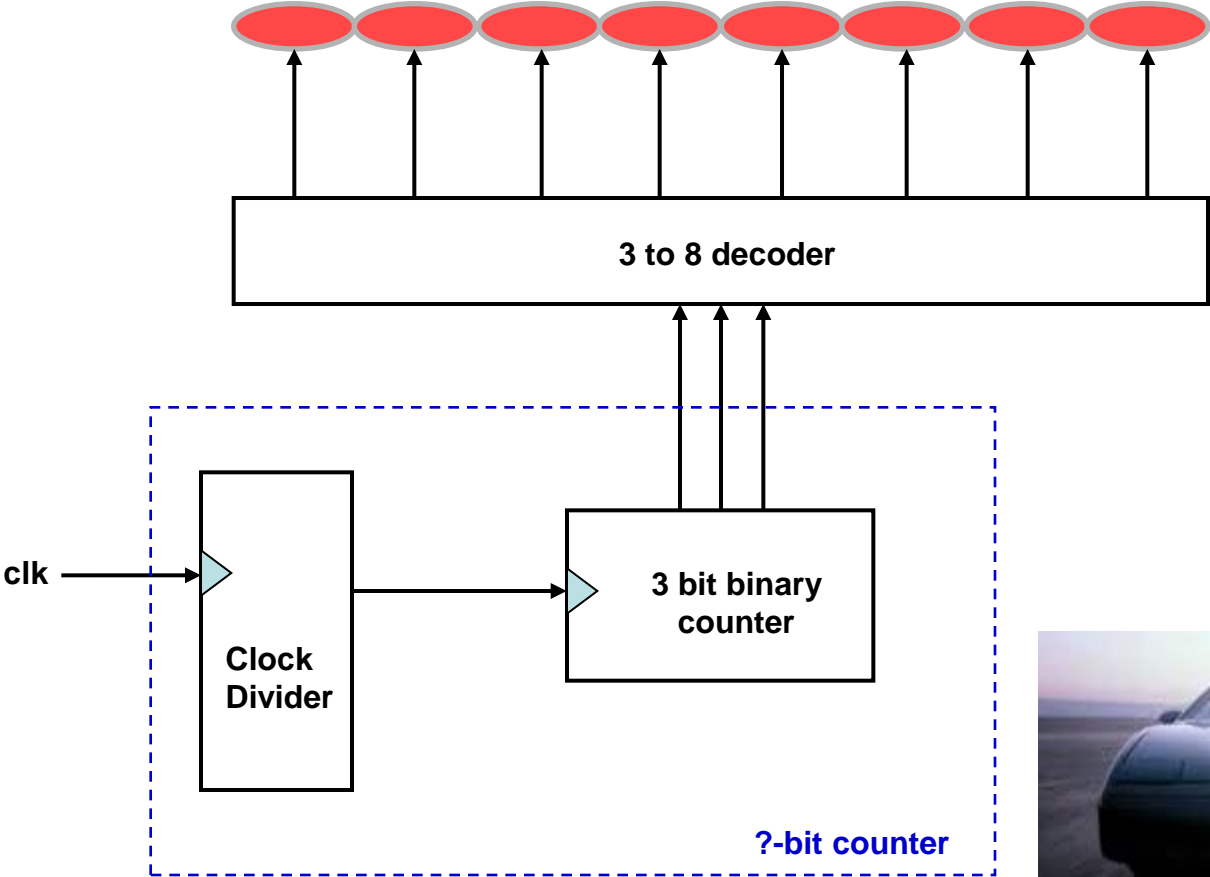

How about *knight rider*?


## Knight-Rider with shift operators

```
architecture KnightRider of KnightRider is
  signal direction: BIT := '0'; -- init is for simulation only
  signal cntr: STD_LOGIC_VECTOR(21 downto 0);
begin
  CLKDIV: process(clk) is begin -- clock divider 50MHz/2^22
    if(RISING_EDGE(clk)) then
      cntr <= cntr +1;
    end if;
  end process; -- can have as many processes as wished

  RIDER: process(cntr(21)) is begin
    if(cntr(21)'EVENT and cntr(21)='1') then -- same as RISING_EDGE
      if(Rst='1') then -- synchronous reset
        LEDES <= (LEDES'LOW=>'1',others=>'0');
      elsif(LEDES(LEDES'LOW)='1') then
        direction <= '1';
        LEDES <= (LEDES'LOW => '0', LEDES'LOW +1 => '1', others=>'0');
      elsif(LEDES(LEDES'HIGH)='1') then
        direction <= '0';
        LEDES <= (LEDES'HIGH => '0', LEDES'HIGH -1 => '1', others=>'0');
      elsif(direction='1') then
        LEDES <= LEDES sll 1; -- sll & srl work for BIT_VECTOR type
      else
        LEDES <= LEDES srl 1;
      end if;
    end if;
  end process;
end KnightRider;
```

```
entity KnightRider is Port (
  clk : in STD_LOGIC;
  Rst : in STD_LOGIC;
  LEDES : inout BIT_VECTOR (7 downto 0));
end KnightRider;
```

# Knight-Rider (another design)

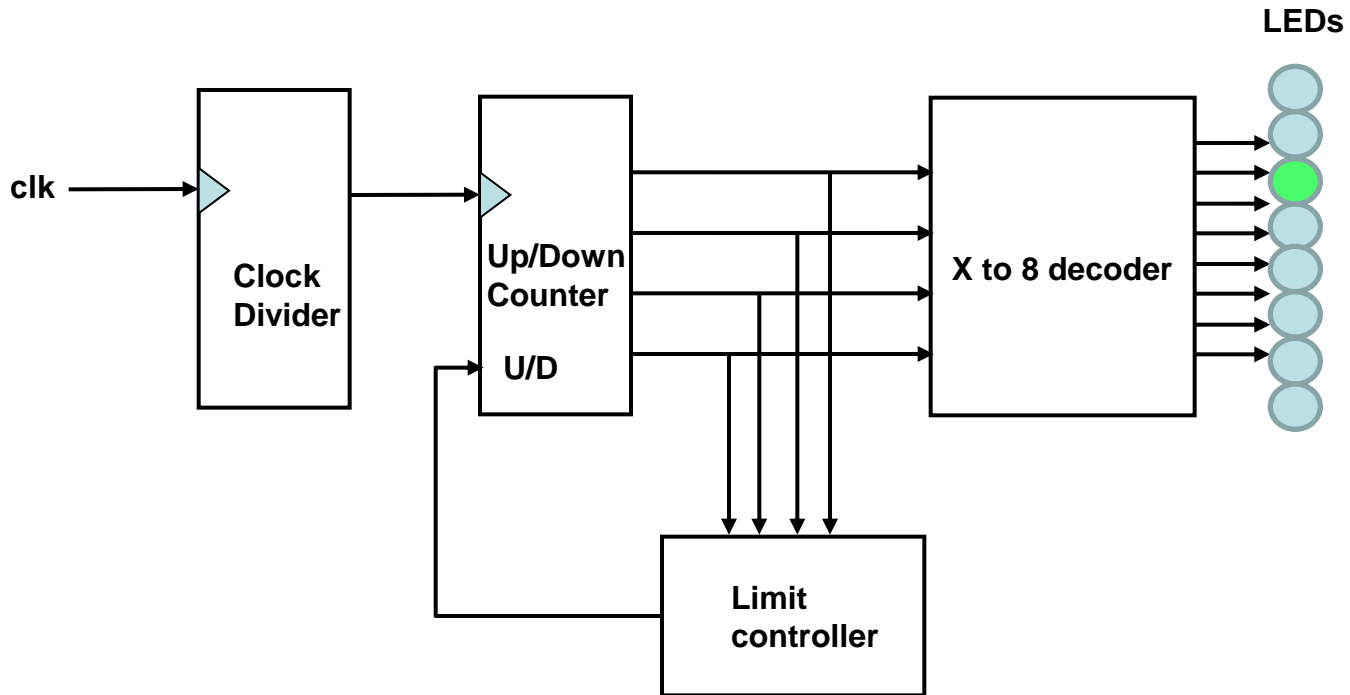

# IEEE Standard Library Packages

numeric\_bit : defines numeric types and arithmetic functions for unsigned & signed bit  
numeric\_std : defines numeric types and arithmetic functions for unsigned & signed std\_logic  
std\_logic\_1164 : some conversions and overloaded logic operators. rising\_edge etc.  
std\_logic\_arith : a set of arithmetic, conversion, and comparison functions  
std\_logic\_misc : supplemental types, subtypes constants, and functions for the Std\_logic\_1164  
std\_logic\_signed : a set of arith., conversion, and comparison functions for STD\_LOGIC\_VECTOR  
std\_logic\_unsigned : a set of unsigned arith., conv., and comp. functions for STD\_LOGIC\_VECTOR  
std\_logic\_textio :  
math\_complex :  
math\_real :

```
FUNCTION rising_edge (SIGNAL s : std_ulogic) RETURN BOOLEAN IS
BEGIN
    RETURN (s'EVENT AND (To_X01(s) = '1') AND
            (To_X01(s'LAST_VALUE) = '0'));
END;
```

```
function max(L, R: INTEGER) return INTEGER is
begin
    if L > R then
        return L;
    else
        return R;
    end if;
end;
```



```
function CONV_INTEGER(ARG: STD_ULOGIC)
return SMALL_INT is
    variable tmp: STD_ULOGIC;
begin
    tmp := tbl_BINARY(ARG);
    if tmp = '1' then
        return 1;
    elsif tmp = 'X' then
        assert false
        report "<message truncated here>"
        severity WARNING;
        return 0;
    else
        return 0;
    end if;
end;
```

Three example functions from std\_logic\_arith and std\_logic\_1164


  
## Signals with Multiple Drivers

**Design** : Inputs `btn1` and `btn2` are connected to S1 and S2 buttons respectively. Buttons are normally open and inputs are pulled-down. Other ends of the buttons are connected to Vcc. S1 button turns a `LED` on whilst S2 turns it off.



### Incorrect Design

```
architecture MultDriven of MultDriven is
begin
```

```
  P1: process(btn1) is begin
        if(RISING_EDGE(btn1)) then
            LED <= '1';
        end if;
    end process;
```

```
  P2: process(btn2) is begin
        if(RISING_EDGE(btn2)) then
            LED <= '0';
        end if;
    end process;
end MultDriven;
```

When you try to synthesize your code, you will get

**ERROR**:Xst:528 - Multi-source in Unit <MultDriven> on signal <LED>  
or something similar.

## Bad Synchronous Description

```
architecture MultDriven of MultDriven is
begin
  process(btn1, btn2) is begin
    if(RISING_EDGE(btn1)) then
      LED <= '1';
    elsif(RISING_EDGE(btn2)) then
      LED <= '0';
    end if;
  end process;
end MultDriven;
```

Try to think of a circuit that is described by the code above.  
Is it possible?


Try to think of a circuit that does what is needed.

# A Working Design

```
architecture SinglyDriven of SinglyDriven is
  signal clk: STD_LOGIC;
begin
  clk <= btn1 or btn2;
  process(clk) is begin
    if(RISING_EDGE(clk)) then
      if(btn1='1') then
        LED <= '1';
      else
        LED <= '0';
      end if;
    end if;
  end process;
end SinglyDriven;
```

← some combinatorial  
← some sequential

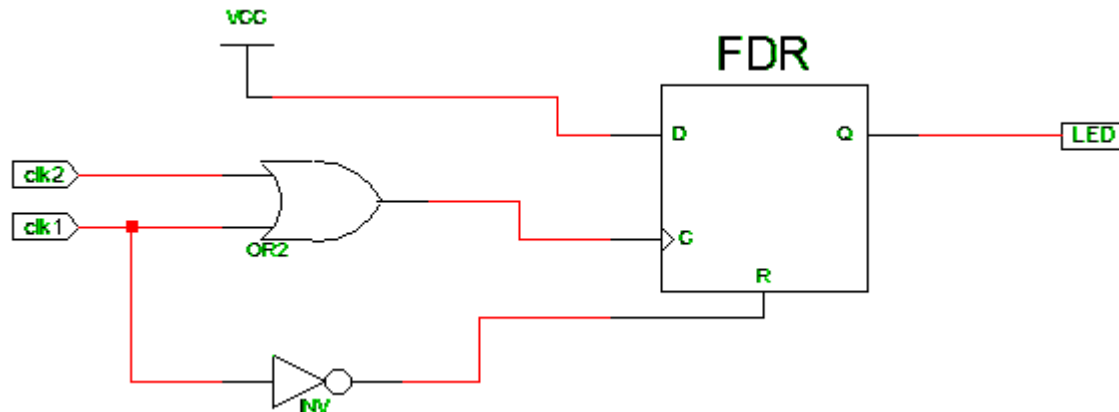
Obviously, when both inputs goes up simultaneously, code lets btn1 to win


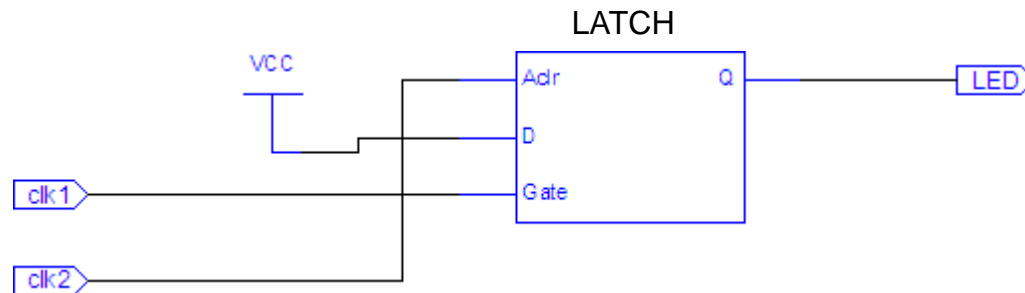
## A Simpler Design

```
architecture SRLatch of SRLatch is
begin
  process(btn1, btn2) is
  begin
    if(btn2='1') then
      LED <= '0';
    elsif(btn1='1') then
      LED <= '1';
    end if;
  end process;
end SRLatch;
```


Synthesizer may complain about inference of a latch. If this is what we want, so we shall ignore the warning here.


 
## Another Simple Design


```
architecture SRasync of SRasync is
begin
  process(btn1, btn2) is
  begin
    if(btn2='1') then
      LED <= '0';
    elsif(RISING_EDGE(btn1)) then
      LED <= '1';
    end if;
  end process;
end SRasync;
```

This line is changed.  
The circuit will look like a simple FF with  
asynchronous reset



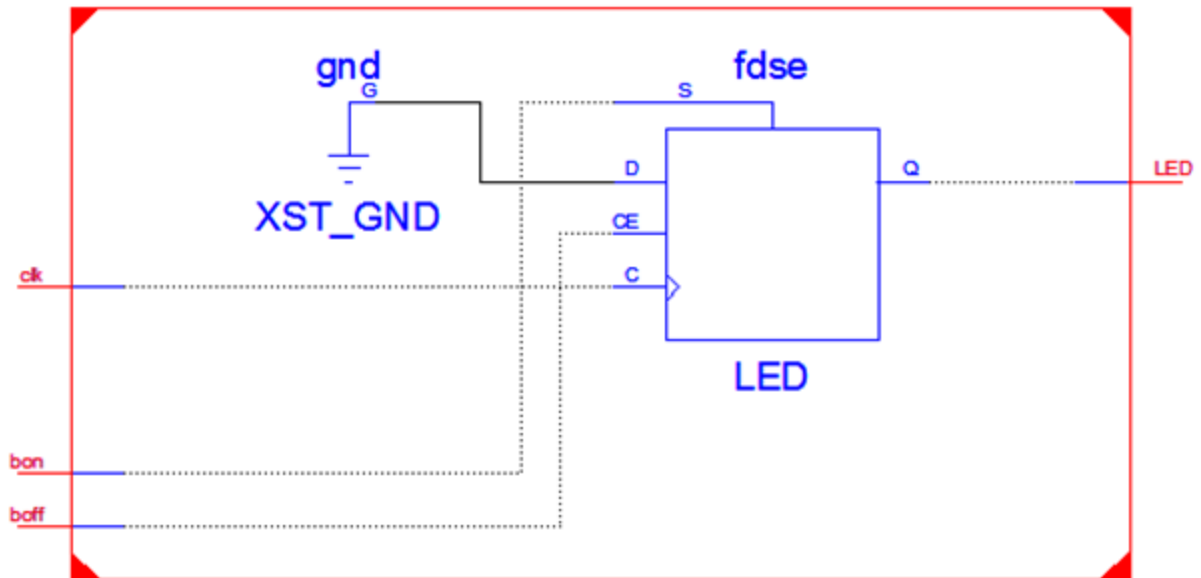
## A Synchronous Design

```
architecture SRSync of SRSync is
begin
  process (clk, bon, boff) is
  begin
    if (RISING_EDGE(clk)) then
      if (bon='1') then
        LED <= '1';
      elsif (boff='1') then
        LED <= '0';
      end if;
    end if;
  end process;
end SRSync;
```


 
## Double Rate Counter

**Design** : Output LEDS (8 bit) counts up one on both rising and falling edge of the single input `clk`.



### Incorrect Design

```
architecture DoubleRate of DoubleRate is
begin
    process (clk) is begin
        if (RISING_EDGE (clk)) then
            cntr <= cntr + 1;
        end if;
    end process;

    process (clk) is begin
        if (FALLING_EDGE (clk)) then
            cntr <= cntr + 1;
        end if;
    end process;
end architecture;
```

When you try to synthesize the code, you will get

`ERROR:Xst:528 - Multi-source in Unit <DoubleRate> on signal <LEDS<7>>`

...


or similar.

## Double Rate Counter - Working Design

```
architecture DoubleRate of DoubleRate is
    signal cntr1: STD_LOGIC_VECTOR(7 downto 0);
    signal cntr2: STD_LOGIC_VECTOR(7 downto 0);
begin
    LEDS <= cntr1 + cntr2; -- + is a valid operator
                          -- for std_logic_vector

    process(clk) is begin
        if(RISING_EDGE(clk)) then
            cntr1 <= cntr1 + 1;
        end if;
    end process;

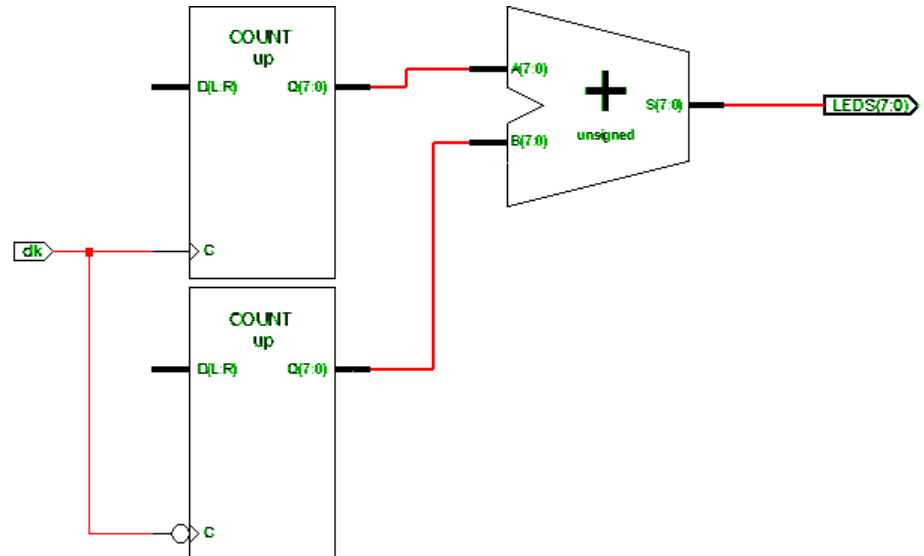    process(clk) is begin
        if(FALLING_EDGE(clk)) then
            cntr2 <= cntr2 + 1;
        end if;
    end process;
end architecture;
```





## Double Rate Counter – Synchronous w/ High Clock

```
architecture DoubleRate of DoubleRate is
    signal Reg: STD_LOGIC;
    signal cntr: STD_LOGIC_VECTOR(7 downto 0);
begin


    process (clkH) is begin
        if (RISING_EDGE (clkH)) then
            if (Reg~=clk) then
                cntr <= cntr + 1;
            end if;
            Reg <= clk;
        end if;
    end process;
end;
```

**Assumption** : rate of the `clkH` is at least twice higher than the rate of the `clk`

**Homework** : Draw the logic circuit you expect before typing in the code.
 
# Variables


**Design** : Calculate the number of ones in an 8 bit signal fed with a clock


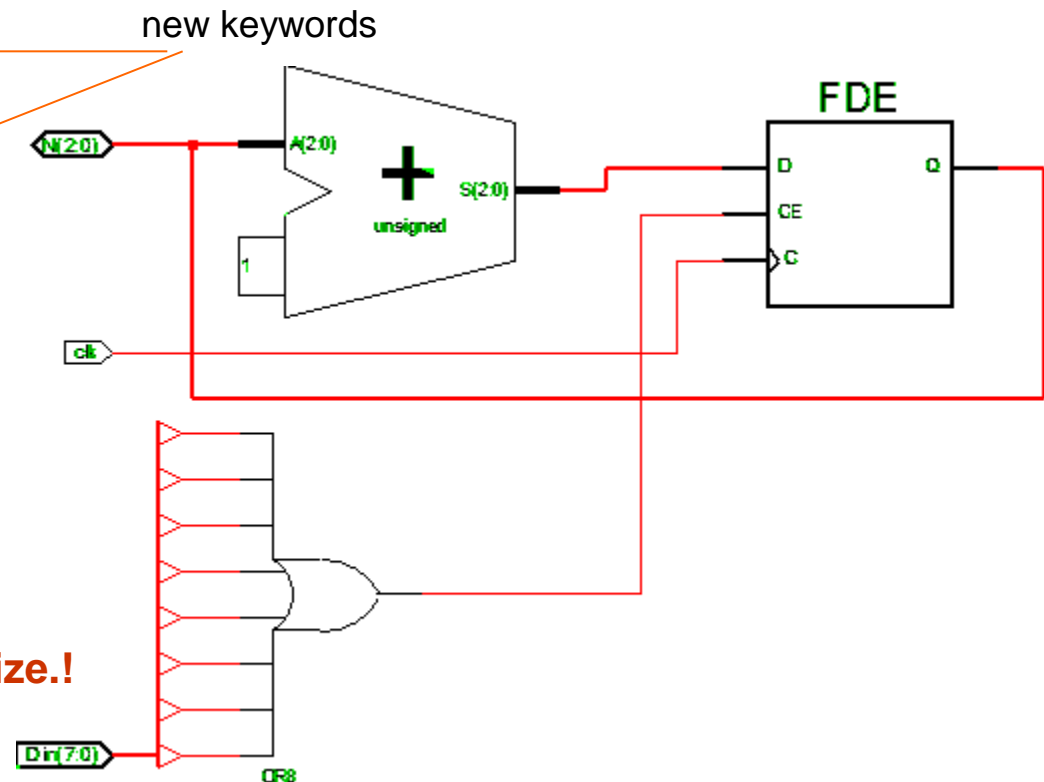
## Incorrect

```
architecture Count1s of Count1s is
begin
  process (clk) is begin
    if (rising_edge (clk)) then
      --N <= "000";
      for i in 0 to 7 loop
        if (Din(i)='1') then
          N <= N + 1;
        end if;
      end loop;
    end if;
  end process;
end Count1s;
```

Putting this will generate "multiple driver" error.



**Incorrect circuit!  
But no warning on synthesizer!**

# Variables


## Correct

```
architecture Count1s of Count1s is
begin
    process (clk) is
        variable T: STD_LOGIC_VECTOR(2 downto 0); -- declared here
    begin
        if(rising_edge(clk)) then
            T := "000"; -- := is used for assignment to variables
            for i in 0 to 7 loop
                if(Din(i)='1') then
                    T := T + 1;
                end if;
            end loop;
            N <= T; -- assignment to variables is immediate
        end if; -- no need to wait for the next clock pulse
    end process;
end Count1s;
```

**Homework** : Design a parity bit calculator. 7 bit input and 8 bit output.

# Resulting circuit

Total of 7 adder and mux stages

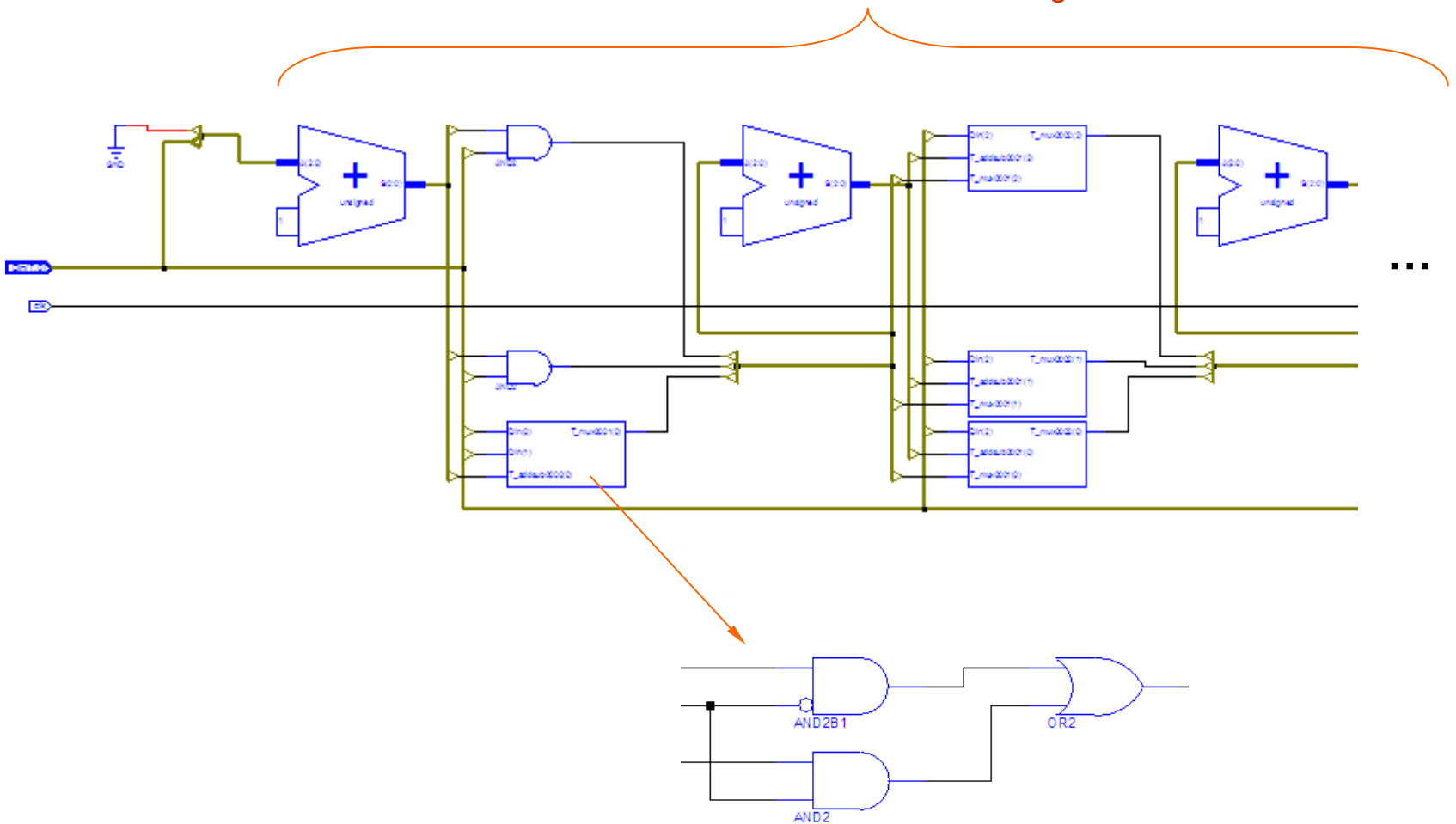

HW: Could it be simpler?

**Homework** : Read sections 5, 6, 7

**Do** problems 5.2, 5.6, 6.1, 6.4, 6.8, 7.2, 7.5.

**Design** an Up-Down counter with Up, Down, clk and Rst inputs.  
It shall not count when Up=Down='0' or Rst='1'.

**END**