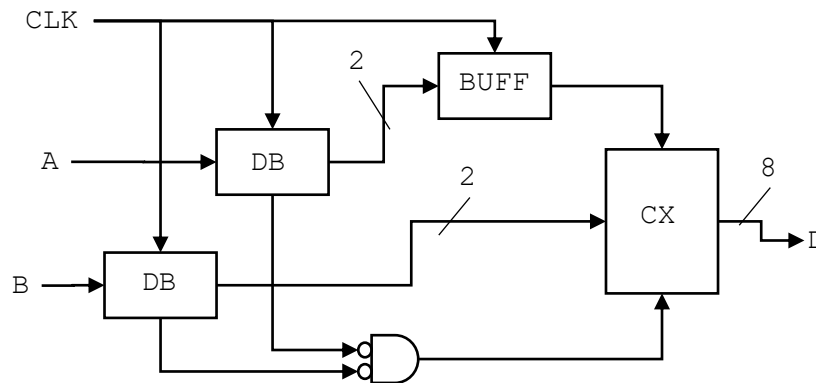


1. Complete VHDL top-level entity for the following block diagram and components.



```

entity MCIR is Port (
  A, B : in  STD_LOGIC;
  D : out STD_LOGIC_VECTOR(7 downto 0);
  CLK : in  STD_LOGIC);
end MCIR;

architecture MCIR of MCIR is
  component DB is port (
    X : out STD_LOGIC_VECTOR(1 downto 0);
    I, CLK : in  STD_LOGIC;
    S : out STD_LOGIC);
  end component;
  component BUFF is port (
    CLK : in  STD_LOGIC;
    X : in  STD_LOGIC_VECTOR(1 downto 0);
    Y : out STD_LOGIC_VECTOR(1 downto 0));
  end component;
  component CX is port (
    XY : in  STD_LOGIC;
    X,Y : in  STD_LOGIC_VECTOR(1 downto 0);
    Z : out STD_LOGIC_VECTOR(7 downto 0));
  end component;

  signal X1, X2, X3 : STD_LOGIC_VECTOR(1 downto 0);
  signal S1, S2, XY : STD_LOGIC;
begin

  XY <= (not S1)and(not S2);
  DB1: DB port map (CLK=>CLK, I=>A, S=>S1, X=>X1);
  DB2: DB port map (CLK=>CLK, I=>B, S=>S2, X=>X2);
  BUFF1: BUFF port map (CLK=>CLK, X=>X1, Y=>X3);
  CX1: CX port map (X=>X2, Y=>X3, XY=>XY, Z=>D);


end MCIR;

```

2. When the input btn1 goes high, output A goes high and stays high for 2 seconds. If btn2 goes high during the first 1 second output B is set to high too. However, if btn2 goes high within the second half of the 2 seconds, output C is set to high. Inputs are disabled after their first rises until the 2 seconds cycle completes. After 2 seconds, all outputs are set to low and inputs are enabled. btn2 has no effect unless the cycle is started by btn1. System operates on a 1 MHz clk input. Design the circuit using VHDL.

```
entity BSEQ is Port (  
    btn1, btn2 : in  STD_LOGIC;  
    A, B, C : out STD_LOGIC;  
    CLK : in  STD_LOGIC); -- 1 MHz  
end BSEQ;  
  
architecture BSEQ of BSEQ is  
    signal cntr: integer range 0 to 2000000;  
    signal Bx, Cx : STD_LOGIC;  
begin  
    B <= Bx; C <= Cx;  
    process(CLK, btn1, btn2, cntr, Bx, Cx) is begin  
        if(rising_edge(CLK)) then  
            if((cntr=0)and(btn1='1')) then  
                cntr <= 1; A <= '1';  
            else  
                if(cntr=2000000) then  
                    cntr <= 0; Bx <= '0'; Cx <= '0';  
                else  
                    cntr <= cntr+1;  
                end if;  
            end if;  
            if((Bx&Cx="00")and(cntr>0)and(btn2='1')) then  
                if(cntr<1000000) then  
                    Bx <= '1';  
                else  
                    Cx <= '1';  
                end if;  
            end if;  
        end if;  
    end process;  
end BSEQ;
```

 3. Design the following 8-bits up-counter using VHDL.



CLK	EN	RST	SET	Q →
x	0	x	x	Q
↑	1	1	x	0...0
↑	1	0	1	D <sub>7</sub> ...D <sub>0</sub>
↑	1	0	0	Q+1

```

entity UPCNT is Port (
    CLK : in  STD_LOGIC;
    D : in  STD_LOGIC_VECTOR(7 downto 0);
    EN, SET, RST : in  STD_LOGIC;
    Q : out STD_LOGIC_VECTOR(7 downto 0));
end UPCNT;

architecture UPCNT of UPCNT is
    signal Qx : STD_LOGIC_VECTOR(7 downto 0);
begin
    Q <= Qx;
    process(CLK,RST,SET,EN,D,Qx) is begin
        if(rising_edge(CLK)) then
            if(EN='1') then
                if(RST='1') then
                    Qx <= (others=>'0');
                elsif(SET='1') then
                    Qx <= D;
                else
                    Qx <= Qx +1;
                end if;
            end if;
        end if;
    end process;
end UPCNT;

```