 


1. Differential Manchester encoding is simply defined as

- No transition at the beginning of bit period indicates a binary 1.
- Transition at the beginning of bit period indicates a binary 0.
- There is a transition in the middle of every bit period.

Timing diagram shows an example Differential Manchester signal generated using a double-rated input clock.



Design a Differential Manchester Encoder circuit using VHDL.


```
entity DME is Port (
    CLKin  : in  STD_LOGIC;
    Din    : in  STD_LOGIC;
    CLKout : inout STD_LOGIC;
    Dout   : inout STD_LOGIC);
end DME;
```

```
architecture DME of DME is
```

```
begin
```

```
    process(CLKin) is begin
        if(falling_edge(CLKin)) then
            CLKout <= not CLKout;
            if(CLKout='1') then
                Dout <= not Dout;
            elsif(Din='0') then
                Dout <= not Dout;
            end if;
        end if;
    end process;
end DME;
```

 2. An 8-bits asynchronous (no clock) ROM with 8 address bits (256-bytes) is serialized out one by one, restarting from the x00 address after xFF.



```

entity Seri is Port (
  clk : in  STD_LOGIC;
  Sout : out STD_LOGIC);
end Seri;

```

```


architecture Seri of Seri is
  type MROM is array (0 to 255) of STD_LOGIC_VECTOR(7 downto 0);
  constant ROM : MROM := (... ROM values here..);
  signal Addr : integer range 0 to 255;
  signal bcnt : integer range 0 to 7;
begin

  process(clk) is begin
    if(rising_edge(clk)) then
      if(bcnt=7) then
        bcnt <= 0;
        if(Addr=255) then
          Addr <= 0;
        else
          Addr <= Addr+1;
        end if;
      end if;
    end if;
  end process;
  Sout <= ROM(Addr)(bcnt);

end Seri;

```

 3. Implement the state machine whose diagram is given in the following figure. Output L depends only on the current state and is 1 only when the state is B. It is zero otherwise. State transitions between B and C do not require any input except clock. A to B transition require x1 and C to A transition require x2 inputs to be 1.



```

entity SM is port (
  clk    : in  STD_LOGIC;
  x1,x2  : in  STD_LOGIC;
  L      : out STD_LOGIC);
end SM;

```

```

architecture SM of SM is
  type state is (A,B,C);
  signal pstate, nstate : state;

```

```

begin
process(clk) is begin
  if(RISING_EDGE(clk)) then
    pstate <= nstate;
  end if;
end process;

```

```

L <= '1' when pstate=B else '0';
process(x1,x2) is begin
  if(pstate=A) then
    if(x1='1') nstate <= B; else nstate <= A; end if;
  elsif(pstate=B) then
    nstate <= C;
  elsif(pstate=C) then
    if(x2='1') then nstate <= A; else nstate <= C; end if;
  else
    nstate <= pstate;
  end if;
end process;

```

```

end SM;

```