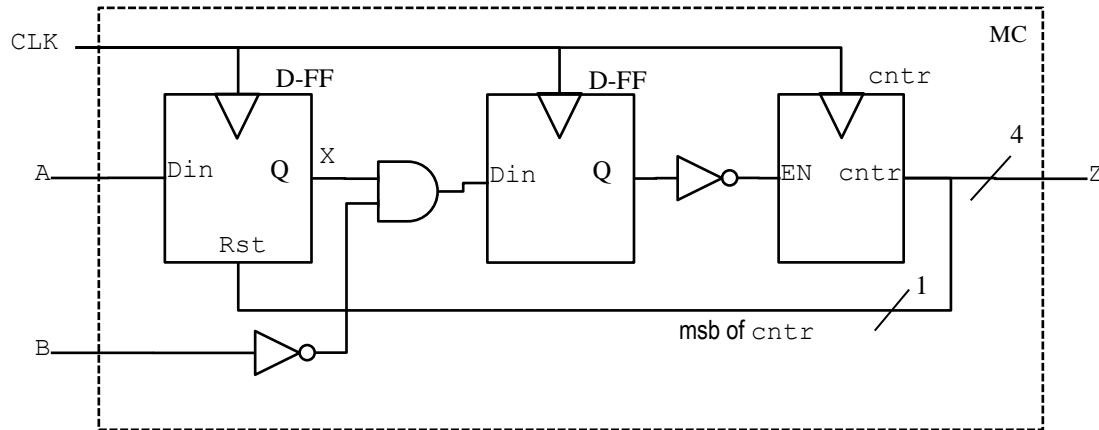


1. Design the following circuit in VHDL within one process. Rst of D-FF is synchronous.




```

entity MC is port (
    clk, A, B : in STD_LOGIC;
    Z : out STD_LOGIC_VECTOR(3 downto 0));
end MC;
architecture MC of MC is
    signal cntr : STD_LOGIC_VECTOR(3 downto 0);
    signal X, Y : STD_LOGIC;
begin
    process(CLK) is begin
        if(rising_edge(CLK)) then
            if(cntr(3)='1') then
                X <= '0';
            else
                X <= A;
            end if;
            Y <= not(X and not(B)); -- see note below
            if(Y='1') then
                cntr <= cntr +1;
            end if;
        end if;
        Z < cntr;
    end process;
end MC;

-- same thing can be achieved with
--     Y <= (X and not(B));
--     if(Y='0') then

```

 2. A counter (`cntr`) counts from 0 to 15, incrementing 1 on every rising edge of `CLK` and going back to zero afterwards, continuously. Another 4-bits counter (`c2`), when enabled through `EN` input, increments when the first counter is "0010" or "1010". Complete this fully synchronous circuit in VHDL.



```


entity CCC is port (
  clk : in  STD_LOGIC;
  EN   : in  STD_LOGIC;
  cnt2 : out STD_LOGIC_VECTOR(3 downto 0));
end CCC;
architecture CCC of CCC is
  signal cntr,c2 : STD_LOGIC_VECTOR(3 downto 0);
begin
  process(CLK) is begin
    if(rising_edge(CLK)) then
      cntr <= cntr +1; -- rollover to 0000 at 1111
      if((EN='1')and((cntr="0010")or(cntr="1010"))) then
        c2 <= c2 +1;
      end if;
    end if;
    cnt2 <= c2;
  end process;
end CCC;

```

 3. In package MyPack.vhd used in your code, an array of records is defined as;

```
type MT is record (M: integer; N: integer);
type MAT is array (integer range <>) of MT;
```

In the following code, an array of MAT type is created along with the component declaration of Cmp. Complete the code that creates a Cmp chain as shown, using for-generate. Each instantiation of Cmp uses corresponding values in the MA array.



```
...
use work.MyPack.All;
entity Test is port (
  CLK : in  STD_LOGIC;
  I : in  STD_LOGIC;
  O : out STD_LOGIC);
end Test;
architecture Test of Test is
  constant MA: MAT(0 to 9):=((5,2), (5,3), (7,6), others=>(1,0));
  component Cmp generic (M: integer; N: integer);
    port ( CLK, I: in STD_LOGIC; O: out STD_LOGIC);
  end component;
  signal Ix : STD_LOGIC_VECTOR(0 to MA'HIGH+1);
begin
  Ix(0) <= I; O <= Ix(MA'HIGH+1)
  L1:for i in 0 to MA'HIGH generate
    Cmp_inst: Cmp
      generic map (
        M => MA(i).M,
        N => MA(i).N
      )
      port map (
        CLK => CLK,
        I => Ix(i),
        O => O(i+1)
      );
  end generate;
end Test;
```

4. Draw the circuit inferred by the following VHDL code, using primitive elements like flip-flops, counters, registers, gates, comparators and basic math-circuits like adders and multipliers.

```

entity Cir is generic ( N: integer:=4); port (
    CLK : in  STD_LOGIC;
    EN  : in  STD_LOGIC;
    Din  : in  integer range 0 to 2**N -1;
    Dout : out integer range 0 to 2**(N+1) -1;
    Str  : out STD_LOGIC);
end Cir;
architecture Cir of Cir is
    signal Dx : integer range 0 to 2**(N+1) -1;
begin
    process(CLK) is
        variable vStr : STD_LOGIC;
    begin
        if(rising_edge(CLK)) then
            vStr := '0';
            if(EN='1') then
                Dx <= Din + Dx;
            end if;
            if(Din>Dx) then
                vStr := '1';
            end if;
            Str <= vStr;
        end if;
        Dout <= Dx;
    end process;
end Cir;

```

--comparator and adder are combinatorial elements

