 


The following is a block diagram of (7,4) error correcting coder circuit with serial-in and serial-out interface.



For each 4-bit input (serial-in) a 8-bit output (serial-out) is generated including additional parity bit. First 4 of these serialized bits are the original input bits, following 3 are codebits and 1 is the even-parity bit. Input bit-rate is half of the output bit-rate. Design the circuit in VHDL.

```
entity SCODER is Port (
    CLK, SIN : in STD_LOGIC;
    SOUT : out STD_LOGIC);
end SCODER;
architecture SCODER of SCODER is
    component HM74 is Port ( -- combinatorial encoder
        HI : in STD_LOGIC_VECTOR(3 downto 0);
        HO : out STD_LOGIC_VECTOR(3 downto 0));
    end component;
    -- your design below --
```

Since input bit-rate is half the output rate and it is not possible to generate 4 bit code (HM74 output) without receiving all 4 bits at the input, we have only two possibilities for implementation;

1. Delay the output until all conversion is done. (requires a 8-bit register before mux)
2. Store previous HM74 output and interlace it with the new input bits. (requires a 4-bit register after HM74)

The following is the first solution;

```
    signal SR,HO : STD_LOGIC_VECTOR(3 downto 0);
    signal HSOUT : STD_LOGIC_VECTOR(7 downto 0);
    signal SEL : integer range 0 to 7 :=0;
begin
    process(CLKI,SIN,SR) is begin -- input shift register
        if(RISING_EDGE(CLKI)) then
            SR <= SIN & SR(3 downto 1);
        end if;
    end process;
    HM74_inst: HM74 port map (HI => SR, HO => HO);
    control: process(CLK,CLKI,SEL) is begin
        if(RISING_EDGE(CLK)) then
            CLKI <= not CLKI; -- for input storage
            if(SEL=7) then SEL <= 0;
            else SEL <= SEL +1;
            if(SEL=0) then HSOUT <= SR & HO; end if;
            -- above is the reg. that stores everything after conversion
        end if;
    end process;
    SOUT <= HSOUT(SEL); -- output mux
end SCODER;
```

The following is the second solution;

```
signal SR,HO : STD_LOGIC_VECTOR(3 downto 0);
signal HSOUT : STD_LOGIC_VECTOR(7 downto 0);
signal HR    : STD_LOGIC_VECTOR(4 downto 0);
signal SEL   : integer range 0 to 7 :=0;
begin
process(CLKI,SIN,SR) is begin -- input shift register
  if(RISING_EDGE(CLKI)) then
    SR <= SIN & SR(3 downto 1);
  end if;
end process;
HM74_inst: HM74 port map (HI => SR, HO => HO);
control: process(CLK,CLKI,SEL) is begin
  if(RISING_EDGE(CLK)) then
    CLKI <= not CLKI; -- for input storage
    if(SEL=7) then SEL <= 0;
    else SEL <= SEL +1;
    if(SEL=0) then HR <= HO; end if;
    -- above is the reg. that stores HM74 output
  end if;
end process;
HSOUT <= SIN & HR(0) & SIN & HR(1) & SIN & HR(2) & SIN & HR(2);
-- It looks like SIN is sent 4 times between HR bits. But its value is
-- changed at every other CLK pulse, so they are different.
-- Current input bits and previous code bits are interlaced.
SOUT <= HSOUT(SEL); -- output mux
end SCODER;
```