 


1. A serial input signal (D) with synchronous clock (CLK) is searched for two binary patterns, one following the other but not necessarily consecutively. Let these patterns, for example, be P0=x"AA" and P1=x"CC". The circuit has three outputs;
A0: set to 1 when P0 is detected.
A1: set to 1 when P1 is detected.
A2: set to 1 when P1 is detected after the detection of P0.
Outputs are set to zero when a reset sequence (Pr=x"01") is detected.
Serial data comes in msb-first. Design the VHDL entity of the circuit.

```
entity SDet is Port (  
    D, CLK : in  STD_LOGIC;  
    A0, A1, A2 : out STD_LOGIC);  
end SDet;  
  
architecture SDet of SDet is  
  
    signal X : STD_LOGIC_VECTOR(7 downto 0);  
    constant P0 : STD_LOGIC_VECTOR(7 downto 0) := x"AA";  
    constant P1 : STD_LOGIC_VECTOR(7 downto 0) := x"CC";  
    constant Pr : STD_LOGIC_VECTOR(7 downto 0) := x"01";  
    signal A0x : STD_LOGIC;  
  
begin  
  
    A0 <= A0x;  
  
    process(CLK) is begin  
        if(rising_edge(CLK)) then  
            X <= X(6 downto 0) & D;  
            if(X=P0) then A0x <= '1';  
            elsif(X=P1) then A1 <= '1';  
                A2 <= A0x; end if;  
            elsif(X=Pr) then  
                A0x <= '0'; A1 <= '0'; A2 <= '0';  
            end if;  
        end if;  
    end process;  
  
end SDet;
```

2. A square wave signal pair will be generated with 90° phase difference between them. Frequency is adjustable by two inputs; Inc for increment Dec for decrement. Increment and decrement are performed at the rising edges of these signals. (*A sentence about limit frequencies is removed from here during the exam in order to reduce confusion*). Design the circuit using VHDL.



```

entity Phased is Port (
    Inc, Dec : in  STD_LOGIC;
    A, B : out STD_LOGIC;
    CLK : in  STD_LOGIC); -- 1 MHz
end Phased;

architecture Phased of Phased is
    signal cntrLim, cntr: integer;
    signal pInc, pDec : STD_LOGIC;
    signal AB : STD_LOGIC_VECTOR(0 to 1);
begin

    A <= AB(0); B <= AB(1);
    process(CLK) is begin
        if(rising_edge(CLK)) then
            pInc <= Inc; pDec <= Dec;
            if((pInc&Inc="01")and(cntrLim<500)) then
                cntrLim <= cntrLim +1;
            elsif((pDec&Dec="01")and(cntrLim>0)) then
                cntrLim <= cntrLim -1;
            end if;
            if(cntr>=cntrLim) then
                case AB is
                    when "00" => AB <= "10";
                    when "10" => AB <= "11";
                    when "11" => AB <= "01";
                    when others => AB <= "00";
                end case;
                cntr <= 0;
            else cntr <= cntr+1;
            end if;
        end if;
    end process;
end Phased;

```


3. A circuit has two de-bounced button inputs and a logic output (to a LED for example). Pressing and releasing the button *b* activates and deactivates the output respectively. However, keeping the button pressed more than 2 seconds locks it. In that case output stays high even after the button is released. Circuit exits the lock-mode when *b* or *s* button is pressed and the output goes low afterwards.

```
entity MCONT is Port (
  CLK : in  STD_LOGIC; -- 1 MHz
  b, s : in  STD_LOGIC; -- buttons
  L : out STD_LOGIC); -- e.g. LED
end MCONT;

architecture MCONT of MCONT is
  constant C2s : integer := 2000000;
  signal cntr : integer range 0 to C2s;
  signal pb, Lx : STD_LOGIC := '0';
begin
```

```
  process(CLK) is begin
    if(rising_edge(CLK)) then
      pb <= b;
      if(s='1') then -- reset condition
        cntr <= 0; Lx <= '0';
      elsif(cntr=C2s) then -- locked case (2sn+)
        if(bp&b="01") then
          Lx <= '0'; -- off but wait for ↓
        elsif(bp&b="10") then -- to reset the counter
          if(Lx='0') then cntr <= 0; end if;
        end if;
      else -- normal operation
        Lx <= b;
        if(b='0') then cntr <= 0;
        else cntr <= cntr +1; end if;
      end if;
    end if;
  end process;
  L <= Lx;
end MCONT;
```

two modes of operation

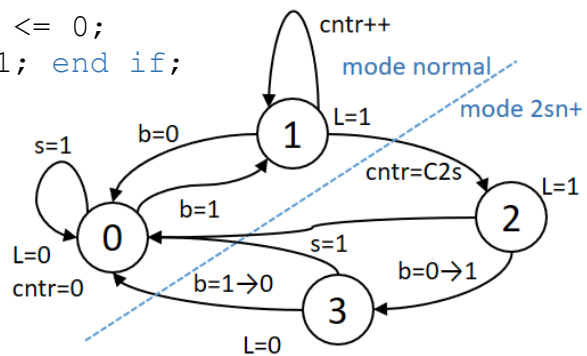

mode 2sn+			
b	s	Lx	cntr
0	0	1	C2s
↑	0	0	C2s
↓	0	0	0
x	1	0	0

normal (cntr < C2s)			
b	s	cntr	Lx
0	0	0	0
1	0	cntr++	1
x	1	0	0

4. A R/W array of records will be created. The record is made of a `std_logic` a `std_logic_vector` of width 8 and an integer ranging from 0 to 127.
- a) The record and array type (of size 512) is declared in a package as follows; (do your own type declarations).

```
type rr is record
  flag : STD_LOGIC;
  data : STD_LOGIC_VECTOR(7 downto 0);
  val  : integer range 0 to 127;
end record;
type MType is array (0 to 511) of rr;
```

- b) Array will be used as a single port memory with address, data and WE connections. Complete the design.

```
entity REC is Port (
  CLK  : in  STD_LOGIC;
  Adr  : in  integer range 0 to 511;
  Din  : in  rr;
  Dout : out rr;
  WE   : in  STD_LOGIC);
end REC;

architecture REC of REC is
  signal Mem : MType;
begin

  process(CLK) is begin
    if(rising_edge(CLK)) then
      if(WE='1') then
        Mem(Adr) <= Din;
      end if;
      Dout <= Mem(Adr);
    end if;
  end process;

end REC;

-- note: depending on the synthesizer capability, one may
-- need to convert & combine record members to
-- STD_LOGIC_VECTOR during read/write operations
-- in order to make use of BRAMs.
```