 


1. Design the following circuit in VHDL within one process. Rst of D-FF is synchronous, cntnr is 4 bits up-counter.




```

entity TL is port (
    clk, Rst, A : in STD_LOGIC;
    Z : out STD_LOGIC_VECTOR(0 to 3));
end TL;
architecture TL of TL is
    signal pA : STD_LOGIC;
    signal cntnr : STD_LOGIC_VECTOR(0 to 3);
begin
    process(CLK) is begin
        if(rising_edge(CLK)) then
            pA <= A;
            if(Rst='1') then
                cntnr <= "0000";
            elsif((cntnr(0)='0')and(pA='0')and(A='1')) then
                cntnr <= cntnr+1;
            end if;
        end if;
        Z < cntnr;
    end process;
end TL;

```

 2. A timer-entity accepts a Start input and outputs a delayed TmOut output. Timer detects the falling-edge of the Start input and starts counting at the rising-edge of the clock CLK. When the count reaches generic integer input DLYCNT, the output TmOut is set to '1' for one clock cycle. Start input is ignored when timer is actively counting. Complete timer circuit in VHDL.



```

entity Timer is
  generic ( DLYCNT : integer := 1000 );
  port (
    clk    : in  STD_LOGIC;
    Start  : in  STD_LOGIC;
    TmOut  : out STD_LOGIC);
end Timer;

architecture Timer of Timer is
  signal cntr : integer range 0 to DLYCNT := 0;
  signal pS   : STD_LOGIC;
  signal counting : STD_LOGIC := '0';
begin
  process(CLK) is begin
    if(rising_edge(CLK)) then
      pS <= Start;
      if(counting='1') then
        if(cntr=DLYCNT-1) then
          counting <= '0';
          TmOut <= '1';
        else
          cntr <= cntr +1;
        end if;
      else
        TmOut <= '0';
        cntr <= 0;
        if((pS='1')and(Start='0'))
          counting <= '1';
        end if;
      end if;
    end if;
  end process;
end Timer;

```

3. Two 4-bits counters up-count in a ping-pong fashion; `cntrA` counts up, while `cntrB` waits at 0000. When `cntrA` reaches 1111, it is set to 0000 and `cntrB` starts counting while `cntrA` waits at 0000. When `cntrB` reaches 1111, it is set to 0000 and `cntrA` starts counting again while `cntrB` waits at 0000. This behaviour continues indefinitely. Design the circuit using VHDL.

```
entity TwoCounters is port (  
    clk : in  STD_LOGIC;  
    A, B : out STD_LOGIC_VECTOR(0 to 3));  
end TwoCounters;  
architecture TwoCounters of TwoCounters is  
    signal cntrA, cntrB: STD_LOGIC_VECTOR(0 to 3);  
    signal AB : STD_LOGIC := '0'; -- which cntr?  
begin  
    A <= cntrA; B <= cntrB;  
    process(CLK) is begin  
        if(rising_edge(CLK)) then  
            if(AB='0') then  
                if(cntrA="1111") then  
                    cntrA <= "0000";  
                    AB <= '1';  
                else  
                    cntrA <= cntrA +1;  
                end if;  
            else  
                if(cntrB="1111") then  
                    cntrB <= "0000";  
                    AB <= '0';  
                else  
                    cntrB <= cntrB +1;  
                end if;  
            end if;  
        end if;  
    end process;  
end TwoCounters;
```